

MAXREFDES1158 Design

The MAXREFDES1158 uses the MAX14946 to provide $2750V_{RMS}$ (60s) of galvanic isolation between the RS-485/RS-422 cable side of the transceiver and the UART side. Both data and power can be transmitted across the isolation barrier in the MAX14946. To achieve data isolation, integrated capacitive isolation allows data transmission between the UART and cable sides of the transceiver. To achieve power isolation, the MAX14946 features an integrated-transformer driver to drive an external center-tapped transformer, that can transfer operating power from the UART side across the isolation barrier to the cable side. In this reference design, the primary side of an external transformer connects to the MAX14946's transformer driver outputs to provide a completed RS-485 isolation solution.

Transformer Selection

The integrated push-pull transformer driver allows the transmission of operating power from the UART side, across the isolation barrier, to the isolated cable side of the device. The 450kHz transformer driver operates with center-tapped primary transformers. Select a transformer with an ET product greater than or equal to the ET of the driver to ensure that the transformer does not enter saturation. E is the voltage applied to the transformer and T is the maximum time it is applied during any one cycle. Calculate the minimum ET product for the transformer primary as follows:

$$ET = \frac{V_{MAX}}{(2 \times f_{MIN})}$$

where V_{MAX} is the worst-case maximum supply voltage on V_{DDA} , and f_{MIN} is the minimum frequency at that supply voltage. For example, when using 5.5V and 350kHz, the required minimum ET product is $7.9V\mu s$. In this reference design, we chose the HanRun HR600755 low cost transformer where $ET = 6 \times 10^{-6}$.

Passive Components on the RS-485 Line

For this reference design, we chose a 120Ω termination resistor. Pullup and pulldown resistors are generally used on the receiver inputs to guarantee a known state if all nodes on the bus are in receive mode or the cable becomes disconnected. Note that the MAX14946 features true fail-safe receiver inputs that ensure RXD is high when the receiver inputs are shorted, open, or connected to an idle bus. We reserved the pullup and pulldown resistor for the customer to test external RS-485 devices without a fail-safe function. We added TVS diodes between the A-B, A-GNDB and B-GNDB lines to enhance protection.

USB to UART Design

The FTDI™ USB to serial UART interface, FT232RL, is used in this design to perform RS-485 communication. For the half-duplex configured RS-485, the transmitter driver and receiver use the same differential line for communication, so the control pin prevents the receiver from receiving the transmitted data from the same device.

Normally, the receiver enable pin is active low, and the transmitter enable pin is active high. We can connect the two pins together so that when the device is in standby mode, the pin is active low, the receiver is enabled and waiting for the data. When the host sends out data, the pin is pulled high to enable the transmitter.

The system block is shown in [Figure 2](#).

Design Resources

Download the complete set of [Design Resources](#) including the schematics, bill of materials, PCB layout, and test files.

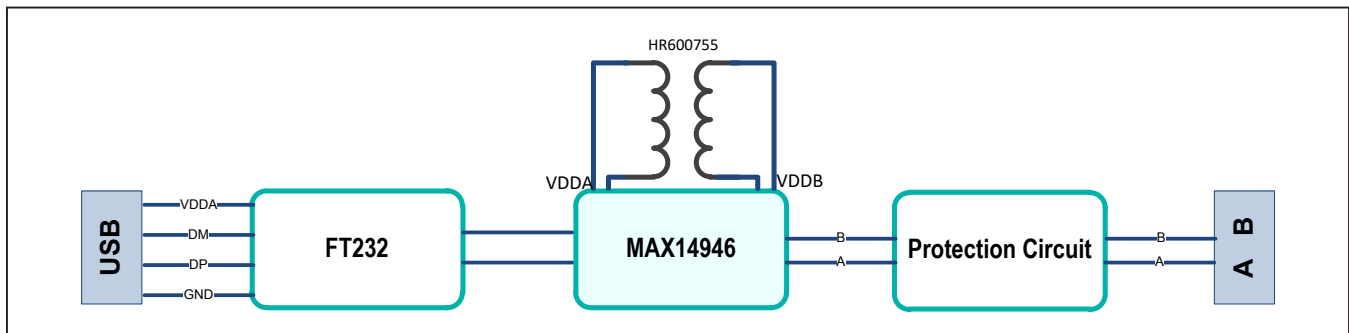


Figure 2. MAXREFDES1158 system block.

FTDI is a registered trademark of Future Technology Devices International Limited.

Revision History

REVISION NUMBER	REVISION DATE	DESCRIPTION	PAGES CHANGED
0	4/19	Initial release	—

Maxim Integrated
www.maximintegrated.com

Maxim Integrated cannot assume responsibility for use of any circuitry other than circuitry entirely embodied in a Maxim Integrated product. No circuit patent licenses are implied. Maxim Integrated reserves the right to change the circuitry and specifications without notice at any time. The parametric values (min and max limits) shown in the Electrical Characteristics table are guaranteed. Other parametric values quoted in this data sheet are provided for guidance.

© 2019 Maxim Integrated Products, Inc. All rights reserved. Maxim Integrated and the Maxim Integrated logo are trademarks of Maxim Integrated Products, Inc., in the United States and other jurisdictions throughout the world. All other marks are the property of their respective owners.